

Code: 23EE3201

**I B.Tech - II Semester – Supplementary Examinations  
DECEMBER 2024**

**ELECTRICAL CIRCUIT ANALYSIS-I  
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70


- Note: 1. This question paper contains two Parts A and B.  
 2. Part-A contains 10 short answer questions. Each Question carries 2 Marks.  
 3. Part-B contains 5 essay questions with an internal choice from each unit. Each Question carries 10 marks.  
 4. All parts of Question paper must be answered in one place.

**PART – A**

1.a)	Define junction.
1.b)	Differentiate between mesh and loop.
1.c)	What role does the coefficient of coupling play in mutual inductance?
1.d)	Define co-efficient of Coupling.
1.e)	Define form factor.
1.f)	Define R.M.S value.
1.g)	Define Q-Factor of a coil.
1.h)	Draw the locus diagram for series RL circuit.
1.i)	Draw the Norton's equivalent circuit.
1.j)	Write the application of Thevenin's theorem.


**PART – B**

					Max. Marks
<b>UNIT-I</b>					
2	a)	State Kirchhoff's Laws.			3 M
	b)	Using Mesh analysis, find the mesh currents in the circuit.			7 M

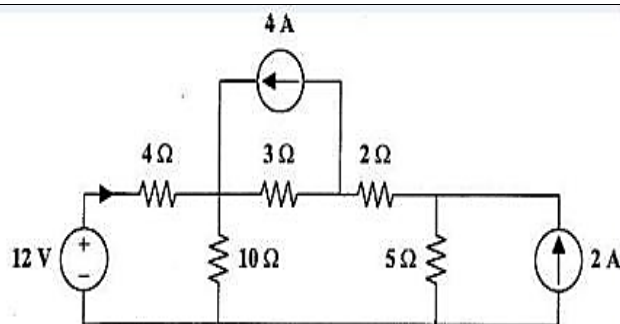

**OR**

- |   |    |                                                                                                                                            |     |
|---|----|--------------------------------------------------------------------------------------------------------------------------------------------|-----|
| 3 | a) | Draw and explain source transformation methods.                                                                                            | 5 M |
|   | b) | Using star - delta transformation, find the equivalent resistance between the terminal's 'A' and 'B' in the network shown in figure below. | 5 M |

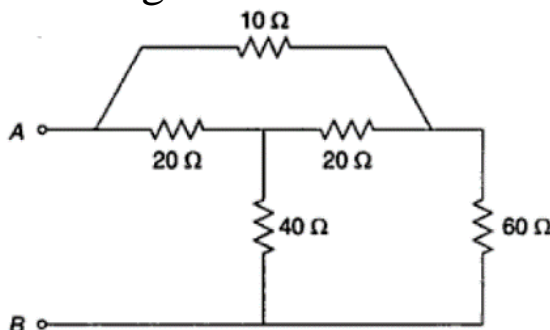

**UNIT-II**

- |   |    |                                                                                                                                                                                                        |     |
|---|----|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----|
| 4 | a) | The essential component of a toaster is an electrical element (a resistor) that converts electrical energy to heat energy. How much current is drawn by a toaster with resistance $12\Omega$ at 110 V? | 3 M |
|   | b) | Compare and contrast the behavior of series and parallel magnetic circuits.                                                                                                                            | 7 M |

**OR**

- |   |    |                                                                                                                                                                                    |     |
|---|----|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----|
| 5 | a) | Two identical coils each have self-inductance 0.03H, if coefficient of coupling $k$ is 0.8, 0.9 and 1 determine the value of mutual inductance (M) between the coils respectively. | 5 M |
|   | b) | Derive the expression for equivalent inductance of two coupled coils connected in parallel aiding.                                                                                 | 5 M |

**UNIT-III**

- |   |    |                                                                              |     |
|---|----|------------------------------------------------------------------------------|-----|
| 6 | a) | Derive the expressions for Average value and RMS value of a sinusoidal wave. | 5 M |
|---|----|------------------------------------------------------------------------------|-----|

	b) A capacitor of capacitance $79.5 \mu\text{F}$ is connected in series with a non-inductive resistance of $30 \Omega$ across $100 \text{ V}$ , $50 \text{ Hz}$ supply. Find (i) impedance (ii) current (iii) phase angle and (iv) equation for the instantaneous value of current.	5 M
--	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----

**OR**

7	a) Find the average and RMS value for the following periodic waveform with amplitude. <div style="text-align: center; margin: 10px 0;"> </div>	5 M
---	------------------------------------------------------------------------------------------------------------------------------------------------	-----

	b) Explain about RLC series circuit with neat diagram.	5 M
--	--------------------------------------------------------	-----

**UNIT-IV**

8	a) Explain how the locus diagram differs in RC circuits with variable resistance and capacitance with neat diagram.	5 M
	b) Explain different types of resonance circuits, and write applications of resonance circuits.	5 M

**OR**

9	In the circuit below, $R = 2 \Omega$ , $L = 1 \text{ mH}$ , and $C = 0.4 \mu\text{F}$ . <ol style="list-style-type: none"> <li>(i) Find the resonant frequency <math>\omega_r</math> and the half-power frequencies <math>\omega_1</math> and <math>\omega_2</math>.</li> <li>(ii) Calculate the quality factor and bandwidth.</li> <li>(iii) Determine the amplitude of the current at <math>\omega_r</math>, <math>\omega_1</math> and <math>\omega_2</math>.</li> </ol> <div style="text-align: center; margin: 10px 0;"> </div>	10 M
---	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------

## UNIT-V

10	a)	Determine current flow in 80 ohms resistance using Thevenin's Theorem	5 M
		b) Explain Superposition theorem with neat diagram.	5 M

## OR

11	a)	Determine current flow in 80 ohms resistance using superposition Theorem.	5 M
		b) Apply Maximum Power Transfer theorem to find the maximum power in R.	5 M